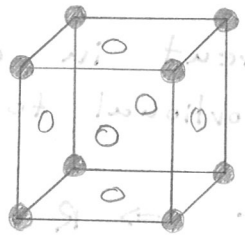


Basic Electronics 2021

- in solid copper Cu atoms are in a face-centered cubic arrangement
- each Cu atom has $29e^-$, $28e^-$ are loosely bound and $1e^-$ is free to dissociate



- conventional current - rate of flow of the charge $+ \rightarrow -$


- conduction speed

$$\text{drift speed } v_d = \frac{dl}{dt}$$

$$v_d = \frac{I}{Ane}$$

$$\text{conduction } e^- \text{ density, } n = \frac{N}{V}$$

$$I = nAv_dq$$

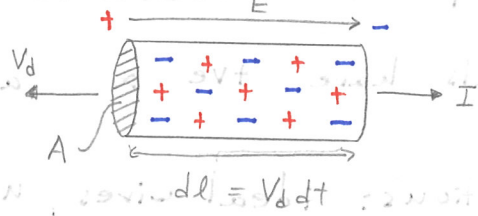

- origin of resistance

↳ charge carriers (free e^-) experience constant acceleration due to the electric field

↳ they undergo collisions with atoms causing them to slow down (don't move in straight line) and travel at average drift velocity

- thermal motion

↳ conductor is not at 0K so random thermal motion of atoms which $\uparrow$ rate of collisions so $\uparrow$ resistance

↳ when e^- collide with atoms it passes on some of its KE resulting in heating of the conductor

- electric potential

↳ potential energy per unit charge $V = \frac{U}{q}$

- potential difference


↳ change in electric potential

$$\Delta V = V_{ab} = V_b - V_a = \frac{U_b - U_a}{q}$$

Ohm's... law

↳ current in a conductor is proportional to the electric field
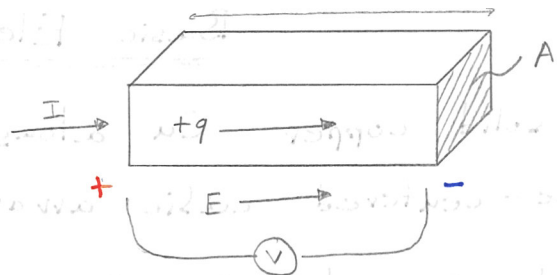
$$J = \frac{E}{\rho} \Rightarrow R = \frac{V}{I} = \frac{\rho l}{A}$$



resistivity and temperature

$$\rho = \rho_0(1 + \alpha(T - T_0))$$

α - temperature coefficient ρ_0 - resistivity at T_0

↳ metals have +ve α and carbon has -ve α

assumptions: ideal wires, no loading, resistance fixed at rtp

electromotive force - EMF

↳ every C of charge gets $\mathcal{E}$ energy as it passes across source

↳ causes the charges to flow by generating E field

- charge in a circuit is always conserved

- real voltage source

↳ finite capacity of energy $V = \mathcal{E} - Ir$

↳ internal resistance r

- ground

↳ electrical potential of our planet defined to be $V=0$

- electrical power

↳ $\mathcal{E}$ is conserved so $\mathcal{E}$ from source must be lost in resistor

$$P = \frac{dE}{dt} = \frac{dE}{dq} \frac{dq}{dt} = VI$$

↳ power in source: $P_S = -\mathcal{E}I = -\frac{\mathcal{E}^2}{R}$


power in resistor: $P_R = \mathcal{E}I = \frac{\mathcal{E}^2}{R}$

- Kirchhoff's voltage law (KVL)

↳ energy is conserved so around one complete

loop charges gain no overall energy

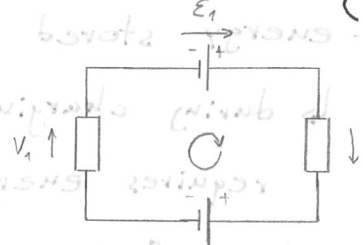↳ $\sum V = 0$ sum of all pd around complete loop is 0




$$\epsilon_1 + \epsilon_2 + V_1 + V_2 = 0$$

- Kirchhoff's current law (KCL)

↳ charge is conserved so at a junction the sum of all current into the junction is 0



↳ $\sum I = 0$

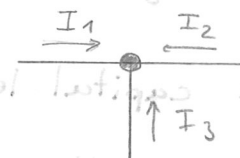

- real measurement devices

↳ real voltmeter - has parallel resistance $r \approx M\Omega$ ideally $r = \infty$

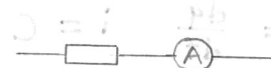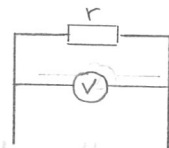
↳ real ammeter - has series resistance $r \approx m\Omega$ ideally $r = 0$



- equivalent resistance

↳ series resistors $R_{\text{series}} = \sum R_i$

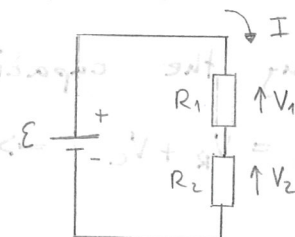↳ parallel resistors $R_{\text{parallel}} = \frac{1}{\sum \frac{1}{R_i}}$



- Voltage divider


$$V_2 = \epsilon \frac{R_2}{R_1 + R_2}$$

- Capacitance

↳ energy stored due to displaced charge

+Q and capacitor remains neutral

$C = \frac{Q}{V}$ holds for any geometry

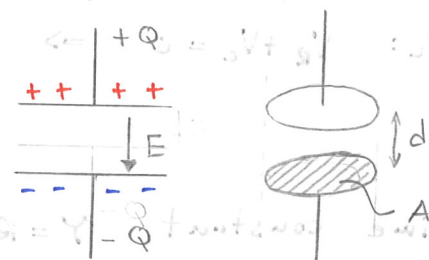

- parallel plate capacitor


$C = \frac{\epsilon_0 \epsilon_r A}{d}$ ϵ_r - relative permittivity of dielectric between plates

- equivalent capacitance

↳ parallel capacitors $C_{\text{parallel}} = \sum C_i$

↳ series capacitors
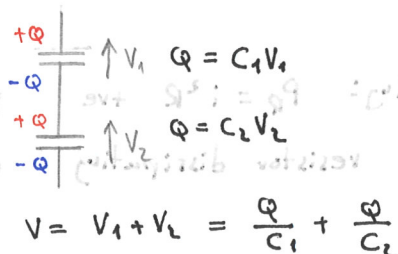
$$C_{\text{series}} = \frac{1}{\sum \frac{1}{C_i}}$$



- energy stored in a capacitor

↳ during charging $q = CV$ so to increase charge $q \rightarrow q + dq$

requires energy $du = Vdq$ and $V = \frac{q}{C}$


$$du = \frac{q}{C} dq \Rightarrow U = \frac{1}{2} C V^2$$

$$\int_0^U du = \int_0^q \frac{q}{C} dq$$

- use capital letters for static quantities and lower case for changing

- current voltage for capacitor
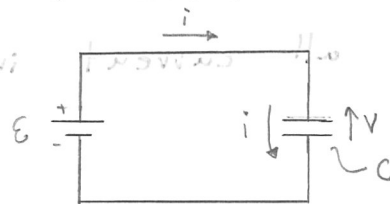
$$q = Cv \quad i = \frac{dq}{dt} \quad i = C \frac{dv}{dt}$$



↳ no charge actually moves through capacitor since dielectric is an insulator. The current is called displacement current


- series RC circuit

↳ charging the capacitor: $t=0 \quad q=0$

$$\text{KVL: } V_s = V_R + V_C \Rightarrow \varepsilon = iR + \frac{q}{C}$$

$$\varepsilon = \frac{dq}{dt} R + q \frac{1}{C}$$
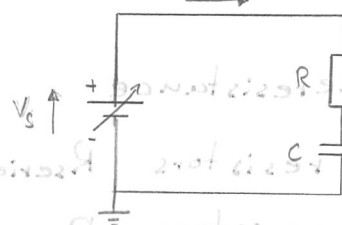
$$q(t) = C\varepsilon (1 - e^{-\frac{t}{RC}})$$



↳ discharging the capacitor: $t=0 \quad q = C\varepsilon$

$$\text{KVL: } V_R + V_C = 0 \Rightarrow 0 = iR + \frac{q}{C}$$

$$= \frac{dq}{dt} R + q \frac{1}{C}$$

$$q(t) = C\varepsilon e^{-\frac{t}{RC}}$$

↳ time constant $\tau = RC$ after 1 time constant the capacitor will always charge up / discharge by 63% of final value ε

- power and energy in RC circuit

↳ charging: $P_R = i^2 R$ +ve
resistor dissipating

$P_C = V_C i$ +ve
capacitor charging

$P_S = -V_s i = -\varepsilon i$ -ve
source delivering E

↳ discharging: $P_R = i^2 R$ +ve
resistor dissipating

$P_C = V_C i$ -ve
capacitor discharging


$P_S = -V_s i = 0$
no source power

$$\frac{P_R}{W} + \frac{P_C}{W} = 1 + 1 = 2$$

$$\frac{1}{C} \int i dt = \frac{1}{C} \int i dt$$

- inductance

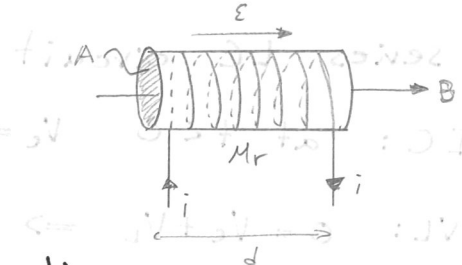↳ changing magnetic flux in coil induces back emf which opposes changes in current



↳ define inductance $L = \frac{\mu_0 \mu_r N^2 A}{d}$ $\mathcal{E} = -L \frac{di}{dt}$


- equivalent inductance

↳ series inductance $L_{\text{series}} = \sum_i L_i$

↳ parallel inductance $L_{\text{parallel}} = \frac{1}{\sum_i \frac{1}{L_i}}$

- energy stored in an inductor

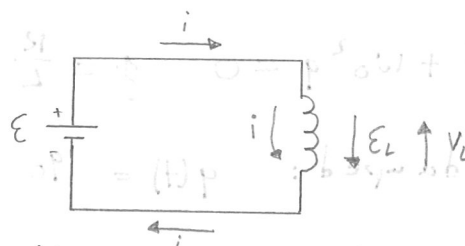↳ $p = V_L i$
 $\frac{dU}{dt} = L i \frac{di}{dt} \Rightarrow U = \frac{1}{2} L I^2$




- current voltage for capacitor $V_L = L \frac{di}{dt}$

- series RL circuit

↳ energizing: $t=0$ $i=0$

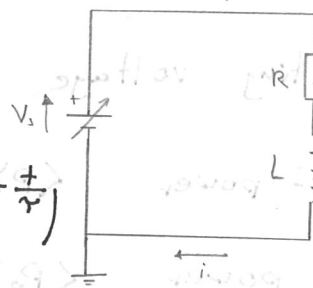kVL: $V_s = V_R + V_L \Rightarrow \mathcal{E} = iR + L \frac{di}{dt}$ $i(t) = \frac{\mathcal{E}}{R} (1 - e^{-\frac{t}{\tau}})$



↳ de-energizing: $t=0$ $i = \frac{\mathcal{E}}{R}$

kVL: $0 = V_R + V_L \Rightarrow 0 = iR + L \frac{di}{dt}$ $i(t) = \frac{\mathcal{E}}{R} e^{-\frac{t}{\tau}}$

↳ define time constant $\tau = \frac{L}{R}$

- power and energy in RL circuit

↳ energizing: $P_R = i^2 R$ +ve resistor dissipating $P_L = V_L i$ +ve inductor energising $P_s = -\mathcal{E} i$ -ve source delivering E


↳ de-energizing: $P_R = i^2 R$ +ve resistor dissipating $P_L = V_L i$ -ve inductor releasing E $P_s = -V_s i = 0$ no source power

- series LC circuit

IC: at $t < 0$ $V_c = \mathcal{E}$ $i = 0$ at $t \geq 0$ $V_c = 0$

KVL: $0 = V_c + V_L \Rightarrow 0 = q \frac{1}{C} + L \frac{dq}{dt}$

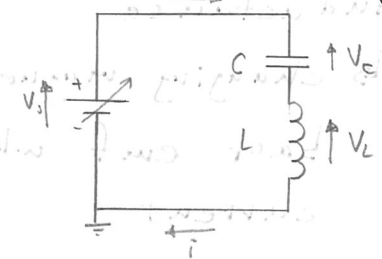gives SHM $q(t) = q_0 \cos(\omega_0 t + \phi)$ $q_0 = C\mathcal{E}$ $\omega_0 = \frac{1}{\sqrt{LC}}$



- damped harmonic oscillator


IC: $V_s = \begin{cases} \mathcal{E} & \text{at } t < 0 \\ 0 & \text{at } t \geq 0 \end{cases}$

KVL: $0 = V_R + V_L + V_c \Rightarrow \dot{q}R + \ddot{q}L + q \frac{1}{C} = 0$

$\ddot{q} + \gamma \dot{q} + \omega_0^2 q = 0$ $\gamma = \frac{R}{L}$ $\omega_0^2 = \frac{1}{LC}$

↳ underdamped: $q(t) = q_0 \frac{\omega_0}{\omega_d} e^{-\frac{\gamma t}{2}} \cos(\omega_d t + \phi)$

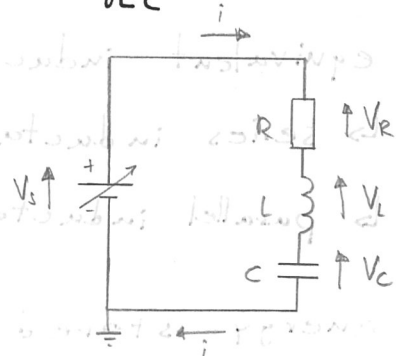↳ critically damped: $q(t) = q_0 (1 + \frac{\gamma t}{2}) e^{-\frac{\gamma t}{2}}$



- alternating voltage $V(t) = V_0 \cos(\omega t + \phi)$ $V_{pp} = 2V_0$ $V_{RMS} = \frac{V_0}{\sqrt{2}}$

- general AC power $\langle P \rangle = V_{RMS} I_{RMS} \cos(\phi)$

- resistor power $\langle P_R \rangle = \frac{1}{2} \frac{V_0^2}{R}$

- capacitor power $\langle P_C \rangle = 0$ provides no E on avg but phase shift $\pm \frac{\pi}{2}$

- phasors

↳ amplitude and phase of oscillating quantities represented as complex quantities

↳ $\tilde{Q}$ is a phasor such that $|\tilde{Q}|$ is amplitude and $\arg(\tilde{Q})$ is the phase

↳ don't forget units

↳ kirchhoffs laws also hold for phasors

- Complex impedance

↳ for any component there is a current $i(t)$ and voltage $v(t)$ oscillating at same ω . write them as $\tilde{I}, \tilde{V}$

↳ impedance $\tilde{Z} = \frac{\tilde{V}}{\tilde{I}}$

- impedance of resistor $\tilde{Z}_R = R$

↳ real value, no phase change, independent of ω

- impedance of a capacitor $\tilde{Z}_C = -\frac{j}{\omega C}$ phase $-\frac{\pi}{2}$

$$V_C(t) = V_0 \cos(\omega t) \quad \tilde{V}_C = V_0$$

$$i(t) = C \frac{dV_C}{dt} = -V_0 \omega C \sin(\omega t) = V_0 \omega C \cos(\omega t + \frac{\pi}{2}) \quad \tilde{I} = V_0 \omega C e^{j\frac{\pi}{2}}$$

- impedance of an inductor $\tilde{Z}_L = j\omega L$ phase $+\frac{\pi}{2}$

$$i_L(t) = I_0 \cos(\omega t) \quad \tilde{I} = I_0$$

$$V_L(t) = L \frac{di}{dt} = -I_0 \omega L \sin(\omega t) = I_0 \omega L \cos(\omega t + \frac{\pi}{2}) \quad \tilde{V}_L = j\omega L$$

- equivalent impedance


↳ series impedance $\tilde{Z}_{series} = \sum_i \tilde{Z}_i$

↳ parallel impedance $\tilde{Z}_{parallel} = \frac{1}{\sum_i \frac{1}{\tilde{Z}_i}}$

- Low pass RC filter

$$\tilde{V}_{out} = \tilde{V}_{in} \frac{\tilde{Z}_C}{\tilde{Z}_R + \tilde{Z}_C} = \tilde{V}_{in} \frac{1}{1 + j\omega CR}$$
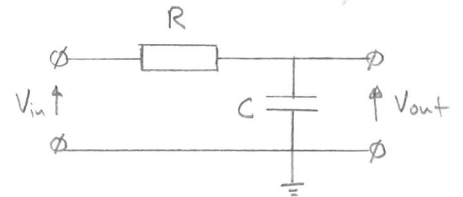
$$\tilde{G} = \frac{\tilde{V}_{out}}{\tilde{V}_{in}}$$




$$\tilde{G} = \frac{1}{1 + j\frac{\omega}{\omega_c}} \quad G = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_c})^2}} \quad \phi = \arg(\tilde{G}) = -\tan^{-1}\left(\frac{\omega}{\omega_c}\right) \quad \omega_c = \frac{1}{RC}$$

- High pass RC filter

$$\tilde{V}_{out} = \tilde{V}_{in} \frac{\tilde{Z}_R}{\tilde{Z}_R + \tilde{Z}_C}$$
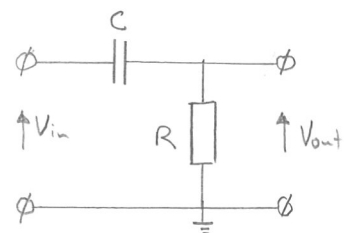
$$G = \frac{\frac{\omega}{\omega_c}}{\sqrt{1 + (\frac{\omega}{\omega_c})^2}} \quad \phi = \tan^{-1}\left(\frac{\omega_c}{\omega}\right)$$



$$\omega_c = \frac{1}{RC}$$


- Low pass RL filter

$$\tilde{V}_{out} = \tilde{V}_{in} \frac{\tilde{Z}_R}{\tilde{Z}_R + \tilde{Z}_L}$$

$$G = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$

$$\phi = -\tan^{-1}\left(\frac{\omega}{\omega_c}\right)$$

$$\omega_c = \frac{R}{L}$$

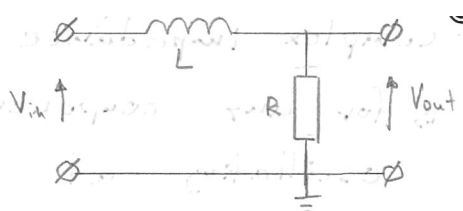


- High pass RL filter

$$\tilde{V}_{out} = \tilde{V}_{in} \frac{\tilde{Z}_L}{\tilde{Z}_R + \tilde{Z}_L}$$

$$G = \frac{\frac{\omega}{\omega_c}}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$

$$\phi = \tan^{-1}\left(\frac{\omega_c}{\omega}\right)$$

$$\omega_c = \frac{R}{L}$$

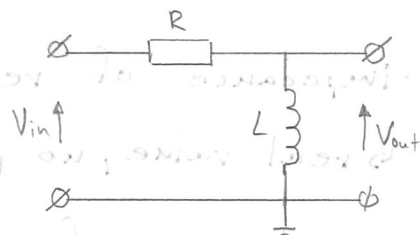

- generally:

↳ Low pass

$$G = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$

$$\phi = -\tan^{-1}\left(\frac{\omega}{\omega_c}\right)$$

$$\omega_c = \frac{1}{RC} = \frac{R}{L}$$

↳ High pass

$$G = \frac{\frac{\omega}{\omega_c}}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$

$$\phi = \tan^{-1}\left(\frac{\omega_c}{\omega}\right)$$

$$\omega_c = \frac{1}{RC} = \frac{R}{L}$$

- comments


↳ filtered frequencies are dissipated as heat in resistor

↳ RC and RL filters have same ω_c they are indistinguishable

↳ $\tilde{Z}_C \propto \frac{1}{\omega}$ so cap passes high frequencies

↳ $\tilde{Z}_L \propto \omega$ so inductor passes low frequencies

- Bode plot

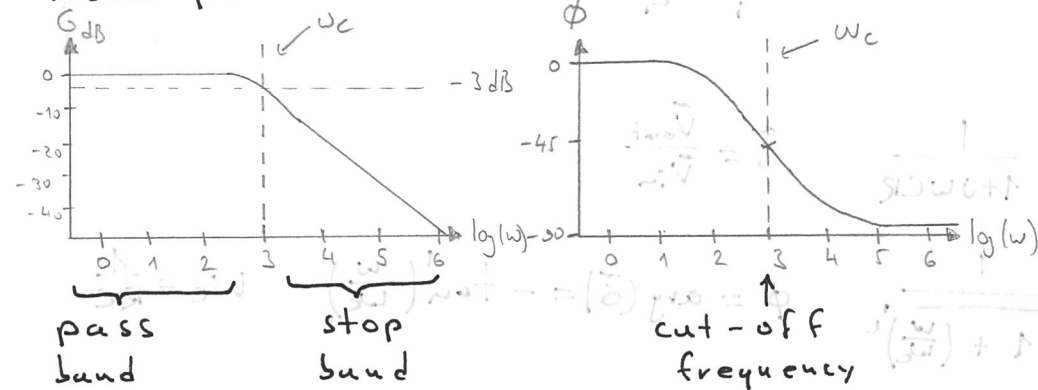

$$G_{dB} = 20 \log_{10}(G)$$

$$\text{at } \omega_c \quad G = \frac{1}{\sqrt{2}}$$

$$G_{dB} = -3.01...$$

$$\left(\frac{\omega}{\omega_c}\right)^{-1} = \phi$$

$$\frac{\omega}{\omega_c} = \phi$$

$$\tilde{V}_{out} = \tilde{V}_{in} \frac{\tilde{Z}_R}{\tilde{Z}_R + \tilde{Z}_L}$$


$$\omega_c = \frac{1}{RC}$$

Series LCR circuit

$$V_s(t) = V_0 \cos(\omega t) \quad \tilde{V}_s = V_0 \quad \tilde{Z} = \tilde{Z}_R + \tilde{Z}_L + \tilde{Z}_C$$

$$= R + j\omega L - \frac{j}{\omega C}$$
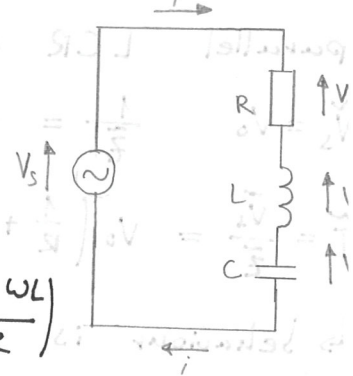
$$\tilde{I} = \frac{\tilde{V}_0}{\tilde{Z}} = \frac{V_0}{R + j\omega L - \frac{j}{\omega C}} \Rightarrow I_0 = \frac{V_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \quad \phi = \tan^{-1}\left(\frac{\frac{1}{\omega C} - \omega L}{R}\right)$$



resonance

↳ at resonance $\tilde{Z}_C = -\tilde{Z}_L$ so cancel out and $\tilde{Z} = R$


↳ $\tilde{I}$ is maximum $\phi = 0$ and $I_0 = \frac{V_0}{R}$

- at low ω Z_L is $\downarrow$ and Z_C $\uparrow$ so Z overall due to capacitor
at high ω Z_L is $\uparrow$ and Z_C $\downarrow$ so Z overall due to inductor

power dissipated in resistor

$$\langle P_R \rangle = \frac{1}{2} R I_0^2$$

as R increases damping increases

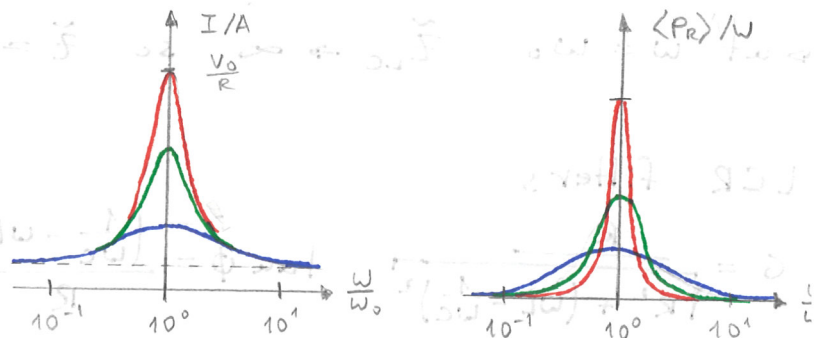

Bandwidth - $\Delta\omega$

↳ at resonance $\langle P_{res} \rangle = \frac{1}{2} R I_0^2$ now set $\langle P \rangle = \frac{\langle P_{res} \rangle}{2}$


$$\Delta\omega = \frac{R}{L} = \gamma \quad \left(\text{solve } |\tilde{Z}| = \frac{1}{\sqrt{2}} \text{ choose } -b + \sqrt{b^2 - 4ac}, +b + \sqrt{b^2 - 4ac} \right)$$

Q factor

↳ dimensionless parameter inversely proportional to strength of damping

$$\text{↳ } Q = \frac{\omega_0}{\Delta\omega} = \frac{\omega_0}{\gamma} \quad \text{for LCR: } Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

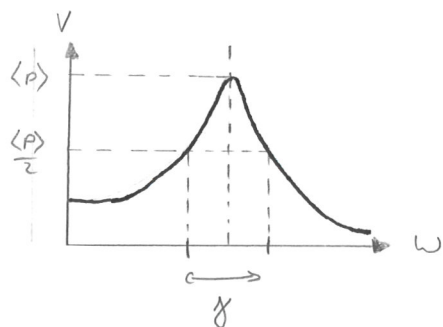
- note resonance curve is not perfectly symmetric





parallel LCR circuit

$$\tilde{V}_s = V_0 \quad \frac{1}{\tilde{Z}} = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$
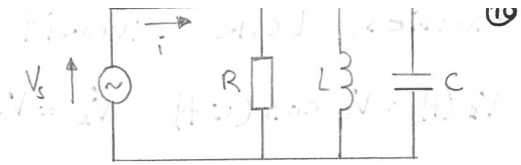
$$\tilde{I} = \frac{\tilde{V}_s}{\tilde{Z}} = V_0 \left(\frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right) \right)$$



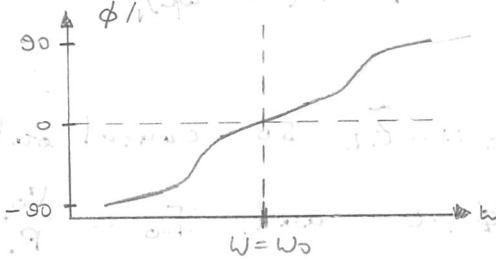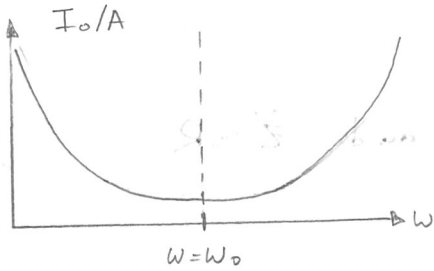↳ behaviour is opposite to series LCR, giving minimum at $\omega = \omega_0$



↳ at low ω $\tilde{Z}_L \rightarrow 0$ so inductor gives high I


at high ω $\tilde{Z}_C \rightarrow 0$ so capacitor gives high I

↳ at $\omega = \omega_0$ $\tilde{Z}_{LC} \rightarrow \infty$ so $\tilde{Z} = R$

- LCR filters



$$G = \frac{R}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$
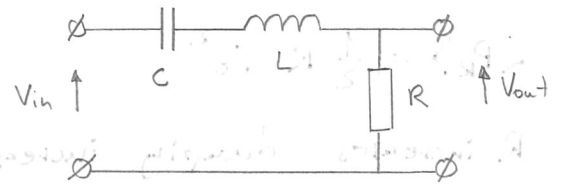
$$\tan \phi = \frac{\left(\frac{1}{\omega C} - \omega L\right)}{R}$$



↳ at $\omega = \omega_0$ $G = 1$ $\phi = 0$ $\tilde{Z}_L = -\tilde{Z}_C$

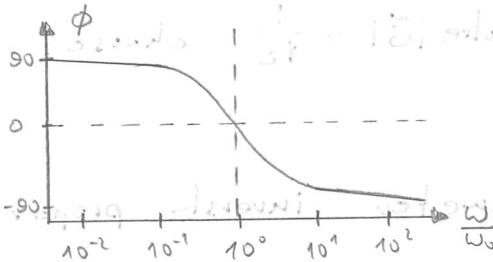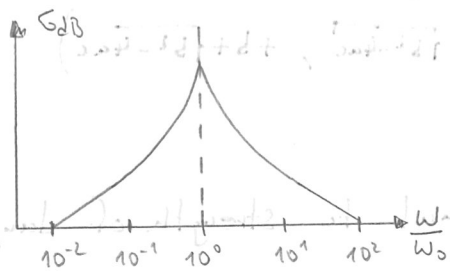at any $\omega \neq \omega_0$ $\left(\omega L - \frac{1}{\omega C}\right)^2$ becomes greater so $G \downarrow$



↳ used in analogue radio tuner. air capacitor adjusted to change ω_0

